

# ECE 215: Circuit Theory and Devices (CTD)

## Mid-Sem Exam (Set B)

Date: October 7, 2024

Duration: 1 hour


Total points: 40 (+7 bonus)

### Instructions

- Write your set in the answer sheet.
- Remember to write units in all your answers.
- Clearly mention the question number you are attempting. Otherwise, zero marks will be given.
- Discussions and calculator sharing are strictly prohibited.

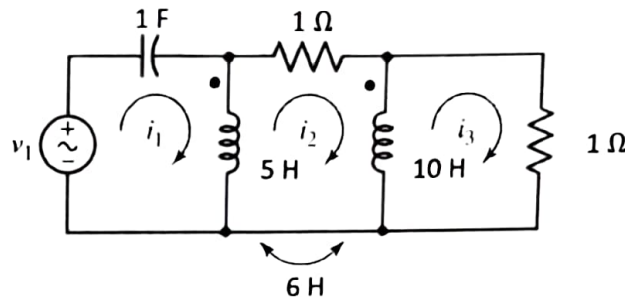
### Questions 1 [CO1, CO2] [5 points]

For the following circuit, write and simplify mesh current equations. (There is no need to find current values).



### Questions 2 [CO1, CO2] [10 points]

Consider the following circuit.

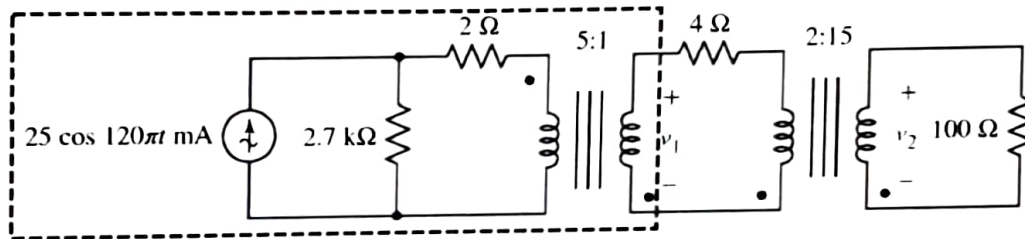

- Find the average power consumed by each resistor. [6 points]
- Determine time-domain voltages  $v_1$  and  $v_2$ . [4 points]
- Find the Thevenin equivalent for the part of the circuit inside the dotted box. [Bonus 4 points]

### Questions 3 [CO1, CO2] [10 points]

A Y-configuration three-phase balanced source is connected to a balanced Y load. The source has positive (also known as "abc") sequence.  $Z_p$  is parallel combination of  $5 - j3 \Omega$  and  $9 + j2 \Omega$  and the line voltage is 300 V.

Assuming zero line resistance, calculate


- Find Power factor of source [2 points]
- Find total power supplied by source [2 points]

$$\frac{731}{197} \quad - \frac{187}{197}$$

Assuming the line resistance of  $1\ \Omega$ , calculate

- (c) Calculate power factor of source [2 points]
- (d) Find total power provided by source [2 points]
- (e) Find total power lost in lines and total power supplied to the load [1+1 points]

Questions 4 [CO1, CO2] [10 points]

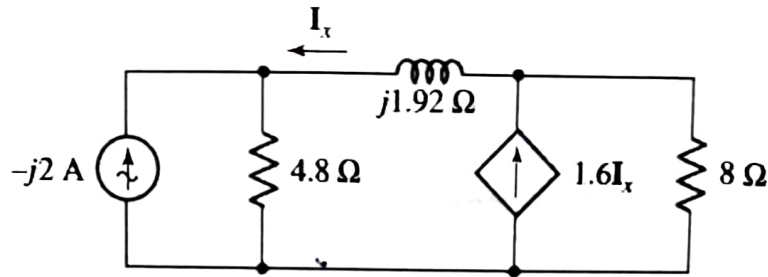

- (a) For each passive element in the circuit, calculate the average power supplied to it. [6 points]
- (b) For each source, determine the average power supplied by it. [4 points]
- (c) Suppose you want to achieve maximum average power delivered to the load  $8\ \Omega$ . You can replace resistor  $8\ \Omega$  with another load. What impedance value will you choose for the new load? [Bonus 3 points]

Questions 5 [CO1, CO3] [5 points]

Use Laplace transform methods to find  $i(t)$  passing through inductor ( $0.2\ \text{H}$ ), which is connected in series with a resistor ( $4\ \Omega$ ) and a voltage source ( $\delta(t) + u(t)\ \text{V}$ ). Assume zero initial conditions.

# ECE 215: Circuit Theory and Devices (CTD)

## End-Sem Exam (Set A)


Date: December 8, 2024	Duration: 2 hours	Total points: 50 (+10 bonus)
------------------------	-------------------	------------------------------

### Instructions

- Write your set in the answer sheet.
- Remember to write units in all your answers.
- Clearly mention the question number you are attempting. Otherwise, zero marks will be given.
- Discussions and calculator sharing are strictly prohibited.

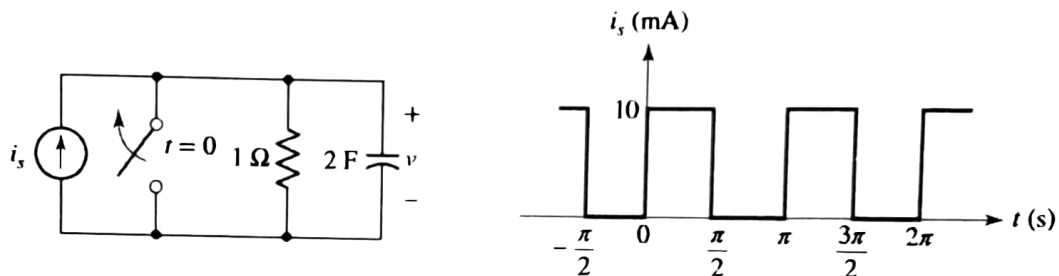
Questions 1 [CO, CO] [10 points]

Calculate  $v(t)$  in a Fourier series representation, if  $i_s(t)$  is given by the below waveform and  $v(0) = 0$ .



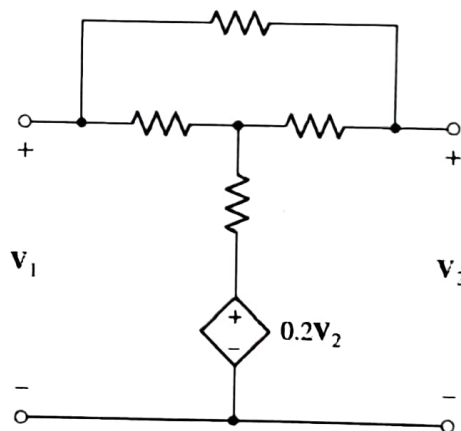Questions 2 [CO, CO] [10 points]

Obtain the impedance parameters of the network shown in the figure. All resistances are  $3\Omega$ .



Questions 3 [CO, CO] [10 points]


Draw the Bode magnitude and phase plot for the following transfer function.

$$H(s) = 1000s / [(s + 1)(10000 + 20s + s^2)]$$

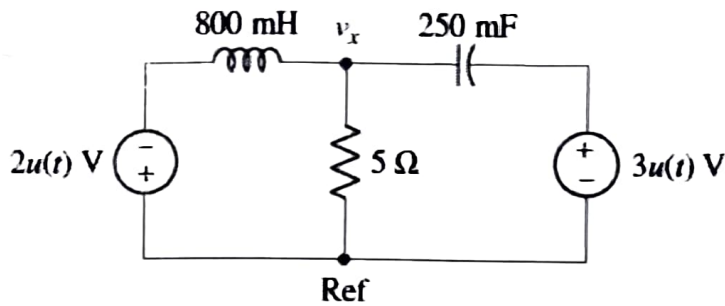Questions 4 [CO, CO] [10 points]

For the circuit shown in the figure,


- Write s-domain nodal equation for  $V_x(s)$ . [5 points]
- Solve for  $v_x(t)$ . [5 points]



Questions 5 [CO, CO] [10 points]

A single-phase three-wire balanced source operates at 50 Hz such that  $V_{AN} = 115$  V. It is connected to a balanced load shown in the figure below.

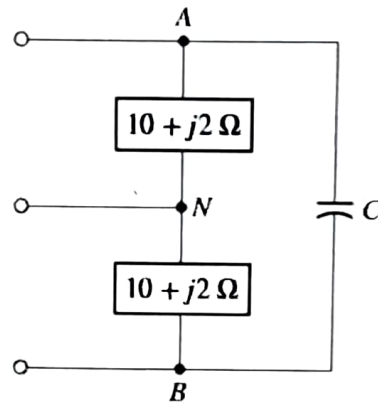- (a) Determine the power factor of the load if the capacitor is omitted [5 points]  
 (b) determine the value of capacitance  $C$  that will achieve a unity power factor for the total load. [5 points]



Question 6 [Bonus 5 points]

For a parallel RLC circuit, show that the half-power bandwidth is inversely proportional to the quality factor.

Question 7 [Bonus 5 points]

Find the Thevenin equivalent of the network as seen by looking into terminals a and b.

